

III B. Tech I Semester Supplementary Examinations, May - 2019**DIGITAL IC APPLICATIONS**

(Common to Electronics and Communication Engineering, Electronics and Instrumentation Engineering, Electronics and Computer Engineering)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answer **ALL** the question in **Part-A**
 3. Answer any **FOUR** Questions from **Part-B**

PART -A

1. a) Define CMOS Logic levels. [2M]
- b) Differentiate between Functions and Procedures in VHDL. [2M]
- c) Explain the library structure of VHDL. [2M]
- d) What are the advantages of ECL? [3M]
- e) Explain about half subtractor. [3M]
- f) Explain a ring counter. [2M]

PART -B

2. a) How that at a given power-supply voltage, an FCT-type I_{CCD} specification can be derived from an HCT/ACT-type C_{PD} specification, and vice versa. [7M]
- b) Quantitatively explain the power dissipation of CMOS circuit. [7M]
3. a) Explain wait, if, case statements in VHDL. [7M]
- b) With an example, explain structural and data flow style of modeling. [7M]
4. a) Explain the blocks inside a logic synthesizer. [7M]
- b) Write a VHDL program for 4x2 Encoder and 2x4 decoder. [7M]
5. a) Write the VHDL architecture for a dual priority encoder. [7M]
- b) Draw the circuit and explain the operation of binary adder-subtractor. [7M]
6. a) Explain the operation of 8bit serial in parallel our shift register and give VHDL description. [7M]
- b) Explain the operation of MOD-10 Counter. [7M]
7. a) Describe about 74x74 D flip-flop and write VHDL program with preset and clear. [7M]
- b) Give a code in VHDL of a serial adder. [7M]
