

**NRT/KS/19/2123**

**Bachelor of Science (B.Sc.) Semester-IV Examination**  
**ELECTRONICS (Analogue & Digital Techniques)**  
**Optional Paper-I**

Time : Three Hours]

[Maximum Marks : 50

**N.B. :**— (1) All questions are compulsory and carry equal marks.  
(2) Draw diagram wherever necessary.

**EITHER**

1. (A) What is feedback ? Explain positive and negative feedback. Draw the block diagram of feedback amplifier and derive an expression for gain of amplifier with feedback. 1+3+6

**OR**

- (B) Explain the construction and working of Colpitts oscillator. A Colpitts oscillator uses the following components in the tank circuit  $L = 100 \text{ mH}$ , and  $C_1 = C_2 = 20 \text{ pF}$ . Calculate the frequency of its output. 6+4

**EITHER**

2. (A) Draw the circuit diagram of monostable multivibrator using OP-AMP and explain its working. Calculate the time delay generated by a monostable multivibrator with  $R = 47 \text{ k}\Omega$ ,  $C = 10 \text{ }\mu\text{f}$ . (Assume that  $R_1 = R_2$ ) 7+3

**OR**

- (B) Explain Symmetrical Astable multivibrator. How is it converted into Asymmetrical Astable multivibrator ? Define duty cycle and state its significance. 6+2+2

**EITHER**

3. (A) Explain the working of weighted resistor type 4-bit DAC with neat circuit diagram. State advantages and disadvantages of it. 7+3

**OR**

- (B) Logic levels for 4-bit R-2R ladder are  $1 = 5\text{V}$  and  $0 = 0\text{V}$ . Calculate output voltage :

(i) (1101)

(ii) Only LSB is 1

(iii) Full scale output.

State the advantages and disadvantages of R-2R ladder type D/A converter. 6+4

**EITHER**

4. (A) What is the need of ADC ? State different types of ADC. Explain construction and working of counter type ADC. State its advantages. 2+6+2

**OR**

- (B) Explain the working of flash type ADC with suitable diagram. State its advantages and disadvantages (any three). 7+3

5. Attempt any **ten** :

(A) What is an oscillator ?

(B) State any two factors affecting the stability of output frequency of an oscillator.

(C) Give the formula for frequency of oscillation in Wein-Bridge oscillator.

(D) State the applications of astable multivibrator.

(E) How many states monostable multivibrator have ?

(F) State the use of instrumentation amplifier.

(G) Define settling time.

(H) State the principle of Dual bias DAC.

(I) Why is it useful to connect an OP-AMP at the output of a DAC ?

(J) State the sampling theorem.

(K) State two advantages of successive approximation type ADC.

(L) What is the role of a comparator in ADC ?

1×10