

**Bachelor of Science (B.Sc.) Semester-IV (CBS) Examination**

**ELECTRONICS**

**(Analogue & Digital Techniques)**

**Paper-I**

Time : Three Hours]

[Maximum Marks : 50

**N.B. :-** (1) All questions are compulsory and carry equal marks.

(2) Draw diagrams wherever necessary.

**1. EITHER**

(a) What is feedback ? Explain the positive and negative feedback. Explain the concept of feedback amplifier.

In a negative feedback amplifier open loop gain is 100,  $\beta = 0.04$  and input voltage  $V_i = 50$  mV, calculate,

(i) Gain with feedback ( $A_f$ )

(ii) Output voltage ( $V_o$ ).

7+3

**OR**

(b) What is oscillator ? Give the classifications of oscillators.

Explain the construction and working of colpitt's oscillator.

1+3+6

**2. EITHER**

(a) With neat circuit diagram explain the construction and working of symmetric astable multivibrator using OP-AMP. Derive the expression for frequency of output of astable multivibrator. 6+4

**OR**

(b) What is Sample and Hold circuit ? Explain the working of S/H circuit using OP-AMP.

Explain the construction and working of instrumentation amplifier.

5+5

**3. EITHER**

(a) What is DAC ? Explain need of DAC with neat circuit diagram, the construction and working of binary weighted 4-bit DAC.

State its limitations.

1+2+5+2

**OR**

(b) Define the following Parameters of DAC :

(i) Resolution

(ii) Accuracy

(iii) Linearity.

Describe the construction and working of R-2R ladder type DAC.

State its advantages.

3+5+2

4. **EITHER**

- (a) What is ADC ? Explain the construction and working of dual slope A/D converter state its advantages and disadvantages. 1+6+3

**OR**

- (b) Describe the construction and working of counter type A/D converter.  
State its advantages and disadvantages. 7+3

5. Attempt any **ten** :

- (a) State any two differences between oscillator and amplifier.
- (b) What are the advantages of negative feedback ?
- (c) What is tank circuit ?
- (d) State the types of feedback used in multi vibrator circuit.
- (e) What are the sources of errors in S/H circuit (any two) ?
- (f) Five the main advantages of instrumentation amplifier.
- (g) State the applications of DAC
- (h) Write the purpose of OP-AMP used in weighted resistor DAC
- (i) What is binary ladder ?
- (j) State the Shannon Nyquist sampling theorem.
- (k) Give the advantages of Flash type ADC
- (l) Define sampling rate of ADC. 1×10