This Question Booklet contains 16 printed pages

Total Marks: 100 Time: 100 Minutes

Candidate's | Seat No.:

Ouestion Booklet Code:

${f A}$	
Seal Sticker	

Candidate's Signature _

Block Supervisor's Signature

DO NOT OPEN QUESTION BOOKLET UNTIL INSTRUCTED.

INSTRUCTIONS FOR CANDIDATE:

- 1. Check Number printed on your OMR SHEET and Question Paper with your SEAT No. before answering the questions. Consult block supervisors in case the above mentioned numbers do not match with your seat number.
- There are total 100 questions. For answer of each question A, B, C, D, E options are given in OMR SHEET. In OMR SHEET, there is "E" option. "E" option is for "Not Attempted". If candidate do not wish to answer the question he/she should select "E" option (Not Attempted). All questions are compulsory.

For Example:

Which state of India has the longest sea shore?

- $A \cap$

- $B \cap C \cap D \cap E \cap$
- (A) Maharashtra
- (B) Tamilnadu
- (C) Gujarat (D) Andhra Pradesh

In this example, the right answer is (C). Therefore, the Circle of (C) has been darkened (encoded). Candidate should not give the answer "Gujarat" in writing.

The options once darkened/answered by candidate cannot be changed.

- 3. Candidates are not permitted to leave examination hall during examination.
- 4. Candidates must strictly enter SEAT NO. in the designated space provided in OMR SHEET as well as Question Paper neatly as soon as they receive the OMR SHEET & Question Paper.
- Candidates must not write name or put any identification sign/symbol on OMR SHEET. In such case strict disciplinary action will be taken against candidate & will be considered disqualified/ineligible. Only Seat No. must be

- entered at designated space provided in OMR SHEET.
- 6. Both, Candidate's & Supervisor's signature must be done on Certificate of OMR SHEET. Unsigned OMR SHEET would not be considered for evaluation
- 7. Candidates are not permitted to use or carry with them any kind of literature, guide, hand written notes, or printed books, mobile phone, pagers, smart watches, camera or any electronic gadgets to examination hall.
- 8. Use of only Non-scientific / Non-programmable calculator shall allow during examination.
- Candidates are not permitted to talk/discuss in the Examination Hall. Any candidate found violating supervisor's instructions will be disqualified.
- 10. Candidates must fully darken circle A, B, C, D and E accordingly with Blue / Black ball pen. If answers are marked with any other coloured ball pen, pencil, white ink (whitner), any corrections are done by candidate by means of blade or rubber or whitner will not be considered for evaluation.
- 11. Candidates may carry QP with them after Examination
- 12. For correct answer 1 (One) marks will be

If candidate gives more than one option as answer for one question in answer sheet (OMR SHEET), or gives wrong answer then the candidate will be allotted Zero (0) marks.

If candidate does not want to answer a particular question and marks (E) or leave the option without encoding on OMR sheet, then no minus marks will be given.

Submit the OMR SHEET to the block supervisor after completion of examination without fail before leaving examination hall, failure to do so will result in disqualification of the candidature for the examination and disciplinary action will be taken against such candidate.

SPACE FOR ROUGH WORK / ૨ફ કામ માટેની જગ્યા

1.	At 300 Kelvin the value of electron concentration is approximately 1.18×10^{10} per cm ³ . T means that roughly electron-hole pairs are to be found in a cube of 10 μ m on a sid	
	(A) 1.18	(B) 11.8
	(C) 0.118	(D) 0.0118
2.		re. If it is doped with Arsenic whose concentration the electron density at room temperature will be
	(A) 10^{21} m^{-3}	(B) 10^{22} m^{-3}
	(C) 10^{23} m^{-3}	(D) 10^{20} m^{-3}
3. The threshold voltage of an n-channel enhancement mode MOSFET is 0.5 V. biased at VGS equal to 3 V. Pinch-off would occur at a drain voltage of		
	(A) 2.5 V	(B) 3.5 V
	(C) 1.5 V	(D) 3 V
4.	The mobility of electrons in a material is exp	ressed with an unit of
	(A) V/sec	(B) m ² /(V.sec)
	(C) m ² /(sec)	(D) $m^3/(V.sec)$
5.	Transition capacitance of a p-n junction diode	with the in reverse bias voltage.
	(A) Increases, increases	(B) Decreases, decreases
	(C) Remains unchanged, decreases	(D) decreases, increases
6. For normal operation of MOSFET, source-substrate and drain-substrate junct and, respectively.		ubstrate and drain-substrate junctions should be
	(A) Forward, Forward	(B) Forward, Reverse
	(C) Reverse, Forward	(D) Reverse, Reverse
7.	IDS - VDS characteristic of p-channel enhance	cement MOSFET falls into quadrant.
	(A) 1 st	(B) 2 nd
	(C) 3 rd	(D) 4 th
8. How many minimum number of NAND gates are required to implement a 2-input E without using any other logic gate?		are required to implement a 2-input Ex-OR gate
	(A) 4	(B) 3
	(C) 5	(D) 6
9.	An n-variable Ex-OR expression is equal to the Boolean function with minterms whose equivalent binary numbers have an number of 1's.	
	(A) $2^{n}/2$, even	(B) $2^{n}/2$, odd
	(C) 2 ⁿ /4, even	(D) $2^{n}/4$, odd
10.	An n-variable Ex-OR and equivalence expressions are when number of variables (n) is	
	(A) same, odd	(B) complement of each other, odd
	(C) same, even	(D) complement of each other, odd or even
11.	A 1-bit full adder circuit can be implemented inputs.	d with and OR gates each with
	(A) One 3×8 decoder, two, two	(B) One 2×4 decoder, two, two
	(C) One 3×8 decoder, two, three	(D) One 3×8 decoder, two, four

Psit College Dekho

14.		as $f = \Sigma(0,2,5,7,8,10,13,15)$? Assume that all the inputs	
	(A) 3	(B) 4	
	(C) 5	(D) 2	
13.	Minimum number of flip-flops requi	red to construct a binary modulo N counter is	
	(A) N	(B) 2N	
	(C) $\log_2(N)$	(D) $2*log_2(N)$	
14.	A 2-input CMOS NAND gate is fabricated in single well CMOS technology. The minimum and maximum supply voltages in the circuit are –VDD and VDD, respectively. The substrate terminal of NMOS are grounded and that of PMOS are connected to VDD. What is wrong with connections of terminals in this circuit which will result into improper functioning of the circuit? (Assume VDD greater than diode cut-in voltage)		
	(A) Connections of substrate termina	al of NMOS to ground	
	(B) Connections of substrate termina	d of PMOS to VDD	
	(C) Connections of substrate termina	d of NMOS to ground and that of PMOS to VDD	
	(D) Nothing wrong with connections		
15.	Which of the following statement is true for the transfer function of band-pass filter?		
	(A) Poles lead zeroes, and the transfer function has two poles and two zeroes.		
	(B) Poles lag zero, and the transfer function has two poles and one zero.		
	(C) Poles lead zeroes, and the transfer function has one pole and two zeroes		
	(D) Poles lag zeroes, and the transfer	function has two poles and two zeroes.	
16.	The bypass capacitor placed in parallel with emitter resistor of common-emitter amplifier can		
	(A) Avoid reduction in gain at all frequencies		
	(B) Avoid reduction in gain at all frequencies except at very high frequencies		
	(C) Avoid reduction in gain at all frequencies except at very low frequencies		
	(D) Doesn't affect frequency respons	se	
17. Race around problem in positive level triggered JK flip flop takes place are and, respectively, and this problem can be avoided i than the propagation delay of JK flip flop. Flip-flop is sensitive clock is ON.		ly, and this problem can be avoided if the clock ON time is	
	(A) 1, 1, greater	(B) 0, 1, lesser	
	(C) 1, 0, greater	(D) 1,1, lesser	
18.	In a microprocessor with 16 address lines, a peripheral is interfaced by using lower four address lines. Peripheral is selected when lower four address lines are at '0'. The address(es) assigned to the peripheral is/are, and this technique of address decoding is called as		
	(A) 00, Absolute decoding	(B) 0000 to FFF0, Absolute decoding	
	(C) 0000 to FFF0, Partial decoding	(D) F0, Partial decoding	
19.	Incorporation of voltage shunt negative feedback in the amplifier circuit results into and in output and input impedances, respectively.		
	(A) Decrease, increase	(B) Decrease, decrease	
	(C) Increase, decrease	(D) Increase, increase	

20.	The unit of phase noise is, and it is the noise power relative to the carrier signal is bandwidth of at certain offset from the carrier.	
	(A) dBm/Hz, 1 Hz	(B) dBc/kHz, 1 kHz
	(C) dBm/kHz, 1 kHz	(D) dBc/Hz, 1 Hz
21.	At the input terminals, lossless short-circuited as inductor for a length, and as capa	stub behaves as open circuited for a length, acitor for a length
	(A) $\lambda/4$, greater than $\lambda/4$, lesser than $\lambda/4$	(B) $\lambda/2$, greater than $\lambda/2$, lesser than $\lambda/2$
	(C) $\lambda/4$, lesser than $\lambda/4$, greater than $\lambda/4$	(D) $\lambda/2$, lesser than $\lambda/2$, greater than $\lambda/2$
22.	Settling time of 2nd order control system is	
	(A) Proportional to the product of "damping	g ratio" and "natural frequency"
	(B) Inversely proportional to the product of	"damping ratio" and "natural frequency"
	(C) Ratio of "damping ratio" to "natural free	equency"
	(D) Ratio of "natural frequency" and "damp	oing ratio"
23.	Which of the following chip is "Programma	ble Priority Interrupt Controller"?
	(A) 8259	(B) 8279
	(C) 8255	(D) 8253
24.	What is the gain of half wave length dipole ant	enna in terms of dBi? Neglect electrical inefficiency.
	(A) 1.76	(B) 1.51
	(C) 5.25	(D) 2.15
25.	Suppose the voltage source can supply 0 to approximate value of the maximum current,	10 V, and has internal resistance of 75 Ω . What is it can provide?
	(A) 133 mA	(B) ∞ A
	(C) 10A	(D) 1.33 mA
26.	In ideal op-amp, the slew rate and G	CMRR are, respectively.
	(A) Infinite, Zero	(B) Infinite, Infinite
	(C) Zero, Infinite	(D) Zero, Zero
27.	The full-scale output of a DAC is 10 mA. If number of required bits are	resolution is to be less than 40 μA , then minimum
	(A) 11	(B) 10
	(C) 8	(D) 9
28.	An analog signal is quantized and transmitted using a PCM system. The tolerable erro sampled amplitude is 0.5% of peak-to-peak full scale value. The minimum binary digits requ to encode a sample is	
	(A) 7	(B) 6
	(C) 5	(D) 8
29.	For a given BJT device, hoe and hie parame	ters can be calculated from
	(A) IB - VBE and IC - VCE, respectively	
	(B) IC - VCE	
	(C) IC - VCE and IB - VBE, respectively	
	(D) IB - VBE	

3 0.	terminals of NMOS transistors are grounded (minimum supply voltage in the circuit) and the PMOS are connected to VDD (maximum supply voltage in the circuit).	
	(A) 2 NMOS transistors	(B) 2 PMOS transistors
	(C) 3 NMOS transistors	(D) 3 PMOS transistors
31.	Which of the following statement is true?	
	(A) Tunnel diode exhibits negative resistanc diodes do not exhibits negative resista	e in its I-V characteristic whereas Gunn and Schottky nce in its I-V characteristic
		negative resistance in its I-V characteristic whereas tive resistance in its I-V characteristic
	(C) Gunn diode exhibits negative resistance diodes do not exhibit negative resistan	in its I-V characteristic whereas Tunnel and Schottky ace in its I-V characteristic
	(D) Gunn, Tunnel and Schottky diodes exh	nibit negative resistance in its I-V characteristic
32.	In a second order system, if the damping ra of roots?	atio is greater than '1', then what would be the nature
	(A) Imaginary	(B) Real and equal
	(C) Real but not equal	(D) Complex conjugate
33.	For M equally likely messages, the averag	e amount of information H is
	$(A) H = \log_{10}(M)$	$(\mathbf{B})\ \mathbf{H} = \log_2(\mathbf{M})$
	$(C) H = 2*log_{10}(M)$	(D) $H = (1/2)*log_{10}(M)$
34.	3 dBi gain of antenna means the direction.	power relative to an isotropic antenna in the peak
	(A) Twice	(B) Thrice
	(C) One half	(D) One third
Identify the region (linear/saturation) of operation for p-channel and n-channel MOS for following cases: (i) p-channel MOSFET with $VT = -1.5 \text{ V}$ and terminal volt values as $VG = 0 \text{ V}$, $VB = 5 \text{ V}$, $VD = 3 \text{ V}$, and $VS = 5 \text{ V}$ and (ii) n-channel MOSFET w V and terminal voltages having values as $VG = 5 \text{ V}$, $VB = 0 \text{ V}$, $VD = 3 \text{ V}$, and $VS = 0 \text{ V}$		ET with $VT = -1.5 \text{ V}$ and terminal voltages having $dVS = 5 \text{ V}$ and (ii) n-channel MOSFET with $VT = 1.5$
	(A) linear, linear	(B) saturation, saturation
	(C) saturation, linear	(D) linear, saturation
Twelve (12) signals each band limited to 5 kHz are to be transmitted over a frequency division multiplexing. If AM - SSB modulation scheme with a guar used, then the bandwidth of the multiplexed signal will be		SB modulation scheme with a guard band of 1 kHz is
	(A) 81 kHz	(B) 51 kHz
	(C) 61 kHz	(D) 71 kHz
37.	2	% above the Nyquist rate. The signal has a bandwidth o 1024 levels. The minimum bandwidth required to
	(A) 72 M bits/sec	(B) 144 M bits/sec
	(C) 72 K bits/sec	(D) 144 K bits/sec

38.	A series tuned antenna circuit consists of a variable capacitor (50 pF to 360 pF) and antenna coil has DC resistance of 12 Ω . The approximate frequency range (f) of radio which the radio is tunable is		
	(A) $2.48 \text{ MHz} < f < 8.4 \text{ MHz}$	(B) $3.4 \text{ MHz} < f < 9.1 \text{ MHz}$	
	(C) $541 \text{ kHz} < f < 1.45 \text{ MHz}$	(D) $436 \text{ kHz} < f < 938 \text{ kHz}$	
39.		nsmitted by binary PCM without compression. If the signal equired to be at least 48 dB, the minimum number of bits	
	(A) 8	(B) 10	
	(C) 12	(D) 14	
40.	N-channel MOSFET device is a good device is a good conductor of digital	conductor of digital level and P-channel MOSFET level	
	(A) 0, 1	(B) 1, 0	
	(C) 1, 1	(D) 0 and 1 both, 0 and 1 both	
41.	The entropy of a message source ge and 0.125 is	The entropy of a message source generating four messages with probabilities 0.5, 0.25, 0.125	
	(A) 1 bit/message	(B) 1.75 bits/message	
	(C) 3.32 bits/message	(D) 5.93 bits/message	
42.	The gain margin of unity feedback sy	ystem $G(s) = 2/[(s+1)(s+2)]$ is dB.	
	(A) 1.76	(B) 3.5	
	(C) -1.76	(D) -3.5	
43.	Consider two signals: x[n] = {1, 2, The index of 1st sample in	-1} and $h[n] = x[n]$. The convolution $y[n] = x[n] * h[n]$ is sequence $x[n]$ is 0.	
	(A) {1, 4, 2, -4, 0}	(B) $\{1, 2, -1\}$	
	(C) {1, 4, 2, -4, 1}	(D) {1, 4, 1}	
44. The closed loop system with transfer function $T(s) = 10/(s^5 + 2s^6)$ and has poles in right half of s-plane.			
	(A) Stable, 0	(B) Unstable, 1	
	(C) Unstable, 3	(D) Unstable, 2	
45.	The open loop transfer function of a	system is	
	G(s)H(s) = K/[s(1+2s)(1+3s)]		
	The phase crossover frequency is		
	(A) 6 rad/sec	(B) 2.46 rad/sec	
	(C) 0.41 rad/sec	(D) 3.23 rad/sec	
46.	A 5V voltage source with internal resistance RS is connected to load resistance of 2 k Ω for a time period of 5 ms. Assume that RS is equal to 3 k Ω in initial 1 ms and after that it takes a value of 8 k Ω . What is the average of current flowing through the load resistance?		
	(A) 0.6 mA	(B) 1.5 mA	
	(C) 0.75 mA	(D) 2.5 mA	

Psit College Dekho

47.	In a series RC circuit with C equal to 1 μ F, the output is taken across C. The phase shift between
	output and input at 20 rad/s is -45°. What is the value of R?

(A) 200 $k\Omega$

(B) 150 $k\Omega$

(C) $100 \text{ k}\Omega$

(D) $50 \text{ k}\Omega$

48. In T flip-flop, the normal and complement outputs of T flip-flop is performed XOR operation and then, connected to the T input of flip-flop. If clock frequency to the circuit is fClk, what is the frequency of the output signal of the circuit?

(A) fClk

(B) fClk/2

(C) fClk/4

(D) 2fClk

49. A 4-bit ripple counter and 4-bit synchronous counter made by flip-flops having a propagation delay of 10 ns each. What is the worst case delay in ripple counter and synchronous counter?

(A) 10 ns, 10 ns

(B) 40 ns, 40 ns

(C) 10 ns, 40 ns

(D) 40 ns, 10 ns

50. In CMOS inverter circuit, as the input signal is swept from 0 V to VDD voltage level, NMOS device moves from ______ to _____ region, and PMOS device moves from _____ to _____ region.

- (A) Cutoff, linear, saturation; cutoff, linear, saturation
- (B) Cutoff, saturation, linear, linear, saturation, cutoff
- (C) Cutoff, linear, saturation, saturation, linear, cutoff
- (D) Cutoff, linear, saturation, cutoff, saturation, linear

51. What is the PIV across each diode of a bridge rectifier with a secondary voltage of 20 V rms?


(A) 14.1 V

(B) 20 V

(C) 28.3 V

(D) 34 V

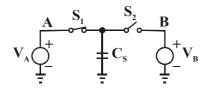52. What is average current flowing in the circuit given below from node A to node B in one clock cycle? Assume switches S1 and S2 are ideal. S1 and S2 are operated by complementary and non-overlapping clock signals. The frequency of clock signals applied to S1 and S2 are fs. Non-overlapping and complementary means when S1 is ON then S2 is OFF, and vice versa. Assume that VA and VB don't change when concerned switch is ON.



 $(A) C_S f_s (V_A - V_B)$

 $(B) (V_A - V_B)/(C_S f_s)$

 $(C) (V_A - V_B)C_S/f_S$

(D) $(V_A - V_B) f_s/C_S$

Contalege Dekho

53. Which of the following functions can be used to generate odd parity for 3-input (x,y,z) bits?

- (A) x (Ex-OR) y (Ex-NOR) z
- (B) x (Ex-NOR) y (Ex-OR) z
- (C) x (Ex-OR) y (Ex-OR) z
- (D) Either of the following functions:
 - (1) x (Ex-OR) y (Ex-NOR) z
 - (2) x (Ex-NOR) y (Ex-OR) z

54. Infinite sheet of charge having charge density ρS C/m ² lying at $x = 0$ and $-\rho S$ C/m ² What is the electric field (E) in the region $0 < x < a$?				
	(A) 0	(B) $(\rho S / \epsilon_0)a_x$		
	(C) $(\rho S / (2 \in 0))a_x$	(D) $(2\rho S / \epsilon_0)a_z$		
55.	The direction of electric field is equipotential surfaces.	to equipotential surface and towards more		
	(A) tangential, positive	(B) normal, negative		
	(C) tangential, negative	(D) normal, positive		
56.	Which of the following represent	s point form of Ampere's circuital law?		
	(A) $\nabla X H = J$	(B) $\nabla X J = H$		
	(C) $\oint H.dL = I$	(D) $\nabla X E = 0$		
57.	value variables m and y at the en	ring statements are part of the program, what would be the d of execution of both statements?		
	m=5;			
	y=m++;			
	(A) $y = 6$, $m = 6$	(B) $y = 5$, $m = 6$		
	(C) $y = 5$, $m = 5$	(D) $y = 6$, $m = 5$		
58.	Two carriers 40 MHz and 80 MHz, respectively, are frequency modulated by a signal of frequency 4 kHz such that the bandwidths of the FM signal in the two cases are the same. The peak deviations in both the cases are in the ratio of			
	(A) 1:4	(B) 1:2		
	(C) 2:1	(D) 1:1		
59.	In c language, use and execution of "continue" statement in while and do loops, transfers control			
		(A) To test condition of while and do loops and then to continue iterative process		
	(B) Next statement after continue statement will be executed			
	(C) Continue statement can't be used in while and do loops			
	(D) Out of while and do loops			
60.	In switch statement of c language, labels.	default case label is and we can have default		
	(A) Optional, multiple	(B) Optional, at most one		
	(C) Mandatory, multiple	(D) Mandatory, at most one		
61.	How many integer data can be st	ored in a variable declared as under in c language?		
	int survey[3][5][12];			
	(A) 180	(B) 312		
	(C) 88	(D) 120		
62.	In c language, the permitted subs following statement is	cript (index) value in height array variable defined as per the		
	float height[50];			
	(A) 1 to 49	(B) 1 to 50		
	(C) 50	(D) 0 to 49		

Psit Colege Dekho

03.	which of the following modulation	scheme has low hoise immunity:	
	(A) PSK	(B) ASK	
	(C) FSK	(D) PSK and FSK, both.	
64.	For a message signal $m(t) = \cos(2\pi f)$ a single side-band signal?	mt) and carrier frequency f _c , which of the following represents	
	(A) $\cos(2\pi f_m t) \cos(2\pi f_c t)$	(B) $\cos(2\pi f_c t)$	
	(C) $\cos(2\pi(f_m + f_c)t)$	(D) $[1+\cos(2\pi f_m t)] \cos(2\pi f_c t)$	
65.	The modulating frequency in FM is increased from 10 kHz to 20 kHz. The bandwidth is		
	(A) Doubled	(B) Halved	
	(C) Increased by 20 kHz	(D) Increased by 10 kHz	
66.		nstruction CMP B has been executed while the content of the register B. As a result, carry flag and zero flag will be,	
	(A) Set, reset	(B) Reset, set	
	(C) Set, set	(D) Reset, reset	
67.	In 8085 microprocessor, the clock fr with 20 T-state is	equency is 5 MHz. The time required to execute an instruction	
	(A) 0.2 μs	(B) 4 μs	
	(C) 2 µs	(D) 0.4 µs	
68.	Consider the execution of following program in 8085 microprocessor.		
	XRAA		
	LXIB, 0007H		
	LOOP: DCX B		
	JNZ LOOP		
	How many times the loop will be executed in above program?		
	(A) 1 time	(B) 7 times	
	(C) 8 times	(D) Infinite times	
69.	The impulse response of a continuo	us-time LTI system is $h(t) = e^{-6t} u(3-t)$. The system is	
	(A) causal and stable	(B) causal but not stable	
	(C) Not causal but stable	(D) Neither causal nor stable	
70.	The impulse response of an LTI sy	stem is $h(t) = u(t) - u(t-4)$. The step response is	
	(A) $tu(t) + (4-t)u(t-4)$	(B) $tu(t) + (1-t)u(t-4)$	
	(C) $1 + t$	(D) $(1+t)u(t)$	
71.	A 4-bit D/A converter produces an output voltage of 4.5 V for an input code of 1001. What will be the value of the output voltage for an input code of 0011?		
	(A) 1 V	(B) 1.5 V	
	(C) 3 V	(D) 0.5 V	
72.	Find parameter h_{21} for a two-port T with a value R.	network. Assume that each branch in T network has resistor	
	(A) -3/2	(B) 1/2	
	(C) -1/2	(D) 3/2	

/3.	3	the input end of the guide, the time taken by the ake c (velocity) as 3×10^8 m/sec.		
	(A) 920 ns	(B) 460 ns		
	(C) 230 ns	(D) 430 ns		
74.	A 0 - 250V voltmeter has a guaranteed accurac percentage of error if it measures 150V?	A 0 - 250V voltmeter has a guaranteed accuracy of 2% of full scale reading. What is the maximum percentage of error if it measures 150V?		
	(A) 2.33%	(B) 3.33%		
	(C) 5.33%	(D) 1.33%		
75.	The smallest change in measured variable to which instrument will respond is			
	(A) Resolution	(B) Accuracy		
	(C) Precision	(D) Resolution and Precision		
76.	The Z transform of u[n] is			
	(A) $1/(1-z^{-1})$, $ z > 1$	(B) $1/(1-z^{-1})$, $ z < 1$		
	(C) $z/(1-z^{-1}), z < 1$	(D) $z/(1-z^{-1}), z > 1$		
77.	A 5 V voltage source is connected to non-inverting terminal of op-amp, 0.1 mA is injected into inverting terminal, and 20 k Ω resistor is connected between inverting terminal and output terminal of op-amp. Calculate output voltage. Assume ideal op-amp.			
	(A) 4 V	(B) 3 V		
	(C) 5 V	(D) 2 V		
78.	In a BJT circuit, I_C = 100 mA and I_E = 100.5 mA. The value of β is			
	(A) 0.995	(B) 201		
	(C) 199	(D) 200		
79.	The both dc load line and ac load line in common-emitter amplifier have the same			
	(A) X-axis intercept	(B) Y-axis intercept		
	(C) Slope	(D) Q-point		
80.	In order to start up and ensure oscillations, it is required oscillator circuit to have phase shift and loop-gain around the feedback loop.			
	(A) Zero degree, greater than or equal to 1			
	(B) 180 degree, less than 1			
	(C) 180 degree, greater than or equal to 1			
	(D) Zero degree, less than 1			
81.	If $u = e^x + y$ and $v = e^x + 7y$, then the Jacobian	$\frac{\partial(x,y)}{\partial(u,v)}$ equals		
	$(A) 7e^x$	(B) 6e ^x		
	(C) 7e ^{-x}	(D) $\frac{e^{-x}}{6}$		

82. 83.	Let $f:[0,1] \to \mathbb{R}$ be continuous function which and $f(1) = 0$. Then which of the following states (A) There exists $c \in (0, 1)$ such that $f(c) = cf(B)$ There exists $c \in (0, 1)$ such that $f'(c) = -f(C)$ There exists $c \in (0, 1)$ such that $f'(c) = cf(D)$ There exists $c \in (0, 1)$ such that $f'(c) = -f(C)$ If $f(x, y) = x^2y - xy^2 + 4xy - 4x^2 - 4y^2$ then $f(C)$ A point of minima $f(C)$ A saddle point	cf'(c) cf'(c) f(c) cf(c)
84.	The improper integral $\int_{0}^{\pi/2} \frac{\sin x}{\sqrt{1-\cos x}} dx$ is	
	(A) divergent	(B) convergent and its value is 0
	(C) convergent and its value is 1	(D) convergent and its value is 2
85.	Let C denote the closed curve in the first qua	drant formed by the parabolas $y^2 = 4x$ and $x^2 = 4y$.
	If the area bounded by C is $\frac{16}{3}$, then the val	
	$(A) \frac{8}{3}$	(B) $\frac{16}{3}$
	(C) $\frac{32}{3}$	(D) $\frac{4}{3}$
86.	The general solution of the equation $y'' + 2y'$	-y=0 is
	(A) $y = e^{-x} \left(c_1 e^{\sqrt{2x}} + c_2 e^{-\sqrt{2}x} \right)$	(B) $y=e^{\sqrt{2}x}(c_1e^x+c_2e^{-x})$
	(C) $y=e^{x}(c_1e^{\sqrt{2}x}+c_2e^{-\sqrt{2}x})$	(D) $y=e^{-\sqrt{2}x}(c_1e^x+c_2e^{-x})$
87.		$\frac{dy}{dx} + y \sin x = e^{\cos x} \text{ is } (f(x) + c)e^{\cos x}, \text{ then } f(x)$
	equals	
	$(A) \sin x$	(B) $\cos x$
	(C) x	(D) 0
88.	The inverse Laplace transform of the function	on $F(s) = \frac{1}{S^2(S^2+1)}$ is
	(A) t cost	(B) t sint
	(C) t – cost	(D) $t - \sin t$
89.	If the Laplace transform of the function f(t) F(0) is	$= \frac{\cos 2t \sin t}{e^t}$ is denoted by F(s), then the value of
	(A) $\frac{-1}{5}$ (C) $\frac{-1}{10}$	(B) $\frac{1}{5}$
	(C) $\frac{-1}{10}$	(D) $\frac{1}{10}$

90. Which of the following is a solution of Laplace equation in two dimensions?		ace equation in two unnensions:
	(A) $e^{-y}\cos x$	(B) $x^2 + y^2$
	(C) $e^{-y} + \cos x$	(D) $x^3 + 3x^2 - 3y^2 + 1$
91.	If the eigen values of the matrix $\begin{bmatrix} a & 1 \\ 1 & 2b \end{bmatrix}$, (volume on which of the following straight lines?	where $a, b > 0$), are 2 and 3 then the point (a, b) lies
	(A) x + y = 5	(B) $x + 2y = 6$
	(C) x + y = 1	(D) x + 2y = 5
92.	Let A be a square matrix of order 3 and sup of linear equations Ax = b has	pose det $A \neq 0$. Then the non-homogeneous system
	(A) no solulion	(B) unique solution
	(C) three solutions	(D) infinite solutions
93.	Let $C = \{ Z : z = \frac{3}{2} \}$. Then the value of the	e contour integral $\int_C \frac{\cos(2\pi z)}{z^2 - 3z + 2} dz$ is
	$(A) -2\pi i$	(B) 2πi
	(C) 1	(D) –1
94.	The coefficient of Z ² in the Taylor series exp	pension of $f(z) = \sin^2 z$ about $z = 0$ is
	(A) 0	(B) 1
	(C) 2	(D) $\frac{1}{2}$
95.	Consider functions $f(z) = \overline{Z}$ and $g(z) = e^{\overline{Z}}$	defined over complex numbers, Then
	(A) f and g both are analytic in C	(B) f is analytic but g is not analytic in C
	(C) g is analytic but f is not analytic in C	(D) Neither f nor g is analytic in C
96.	Bag A contains 2 white and 3 red balls and Bag B contains 4 white and 5 red balls. One ball drawn at random from one of the bags and it is found to be white. What is the probability the white ball is drawn from Bag B?	
	(A) $\frac{9}{19}$	(B) $\frac{18}{19}$
	(C) $\frac{5}{19}$	(D) $\frac{10}{19}$
97.	The probability of obtaining at least two 'Fi	ive' in rolling a fair die 3 times is
	$(A) \frac{2}{9}$	(B) $\frac{1}{9}$
	(C) $\frac{2}{27}$	(D) $\frac{1}{27}$

- 98. If the mean of the 15 observations is $x_1, x_2,, x_{14}, x_{15}$ is 15 then the mean of the 15 observations $y_1, y_2,, y_{14}, y_{15}$ (where $y_i = x_i + i$ for i = 1, 2,15) is
 - (A) 23

(B) 22

(C) 11

- (D) 9
- 99. Which of the following iteration formula is suitable for computing the cube-root of the number 11?
 - (A) $x_{n+1} = \frac{x_{n}^{3} + 11}{2x_{n}^{2}}$

(B) $x_{n+1} = \frac{3x_n^3 + 11}{2x_n^2}$

(C) $x_{n+1} = \frac{2x_{n}^{3} + 11}{3x_{n}^{2}}$

- (D) $x_{n+1} = \frac{x_{n}^{3} + 11}{3x_{n}^{2}}$
- 100. Which of the following is a single step method for numeric solution of ordinary differential equations?
 - (A) Gauss Jordan method

(B) Secant method

(C) Runge - Kutta method

(D) Bisection method



SPACE FOR ROUGH WORK / રફ કામ માટેની જગ્યા